

计算机学院专业必修课

---

# 计算机组成

多周期MIPS：数据通路/控制  
时序逻辑：状态机

高小鹏


北京航空航天大学计算机学院  
系统结构研究所

# 提纲

- 内容主要取材
  - 数字设计和计算机体系结构（第3章，第7章）
- 多周期数据通路控制信号分析
- 多周期控制器状态机构造
- 多周期性能分析
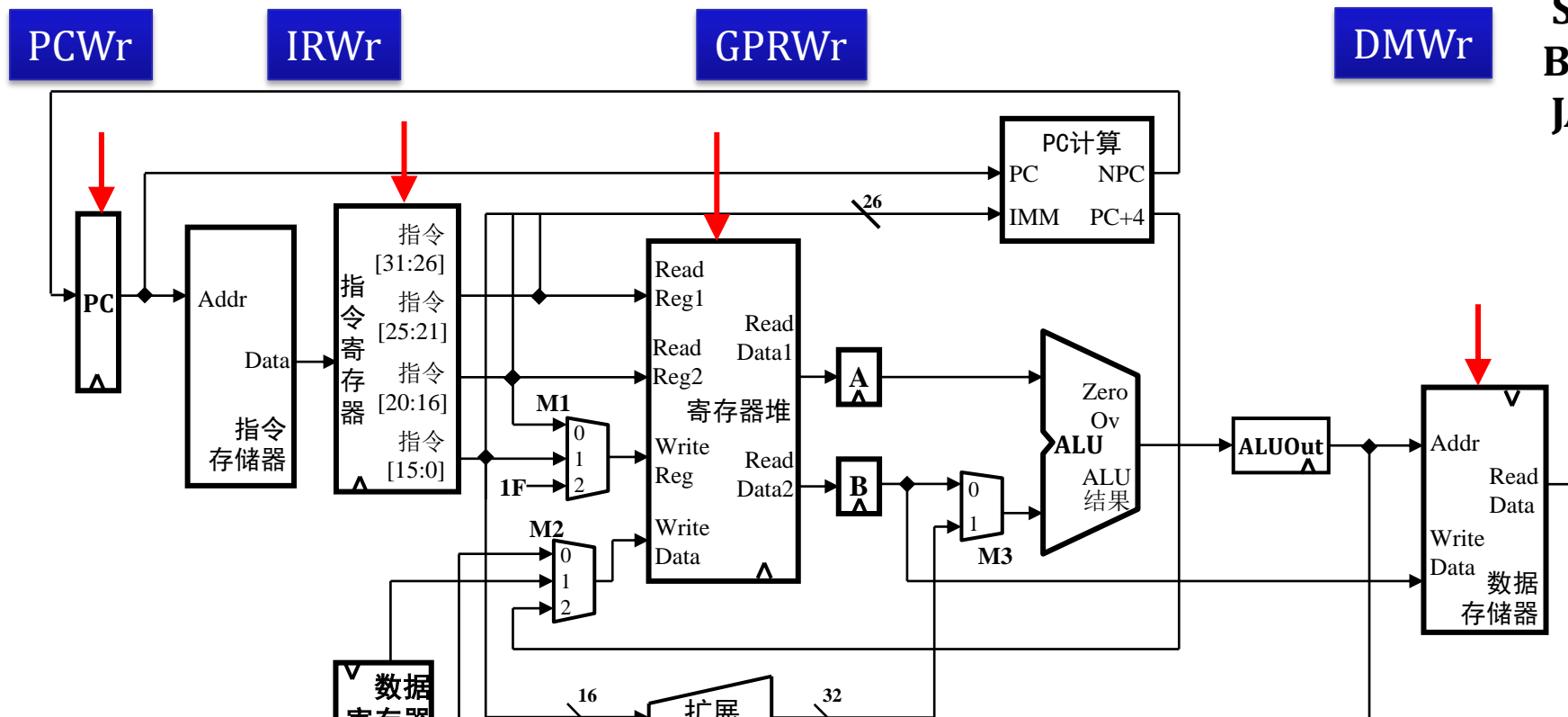
# 多周期数据通路控制信号：寄存器写使能

LW  
ADDU  
SUBU  
ORI  
LUI  
SW  
BEQ  
JAL




## 写使能信号

1: 允许写入; 0: 禁止写入

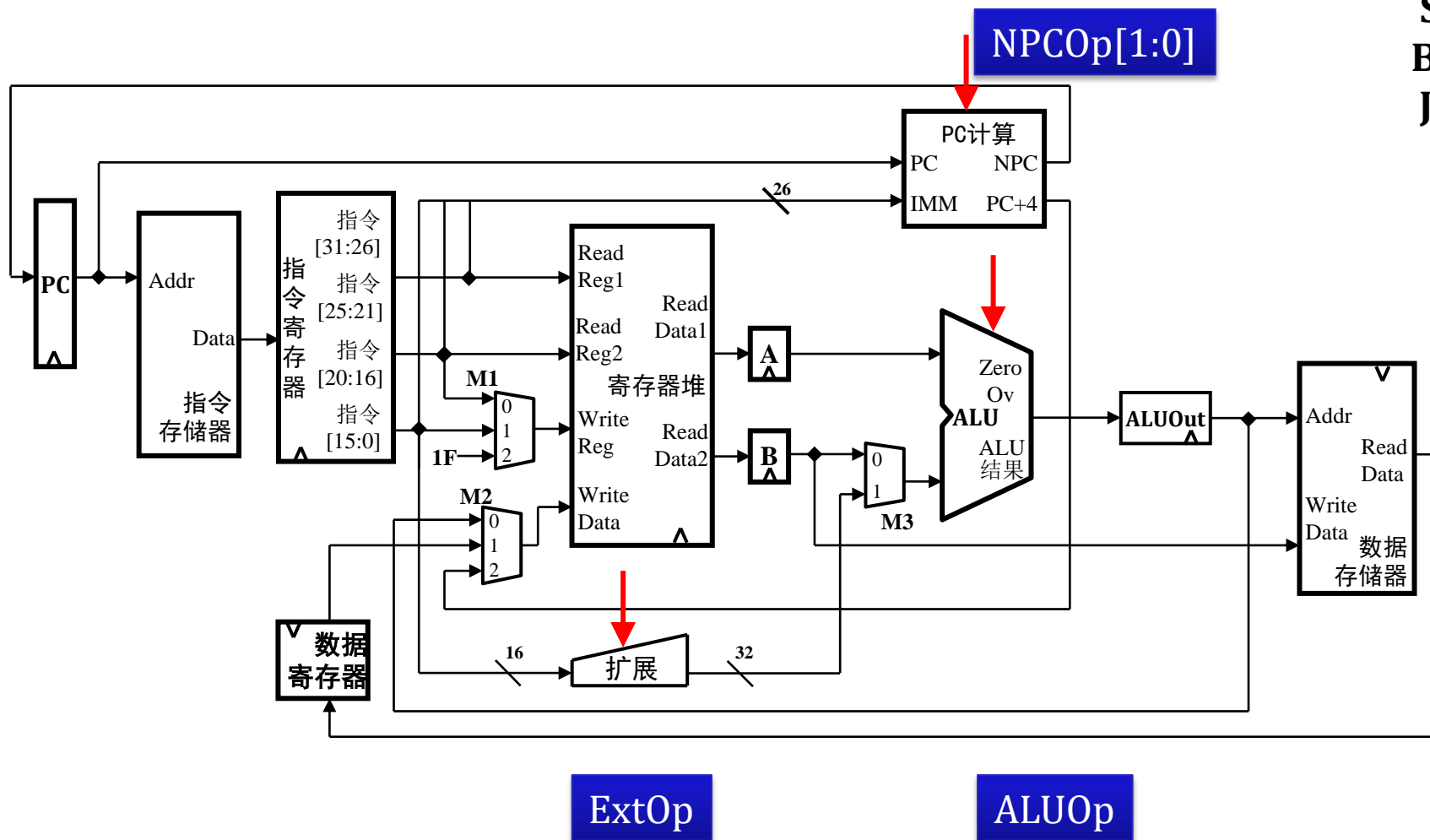
# 多周期数据通路控制信号：操作选择

LW  
ADDU  
SUBU  
ORI  
LUI  
SW  
BEQ  
JAL


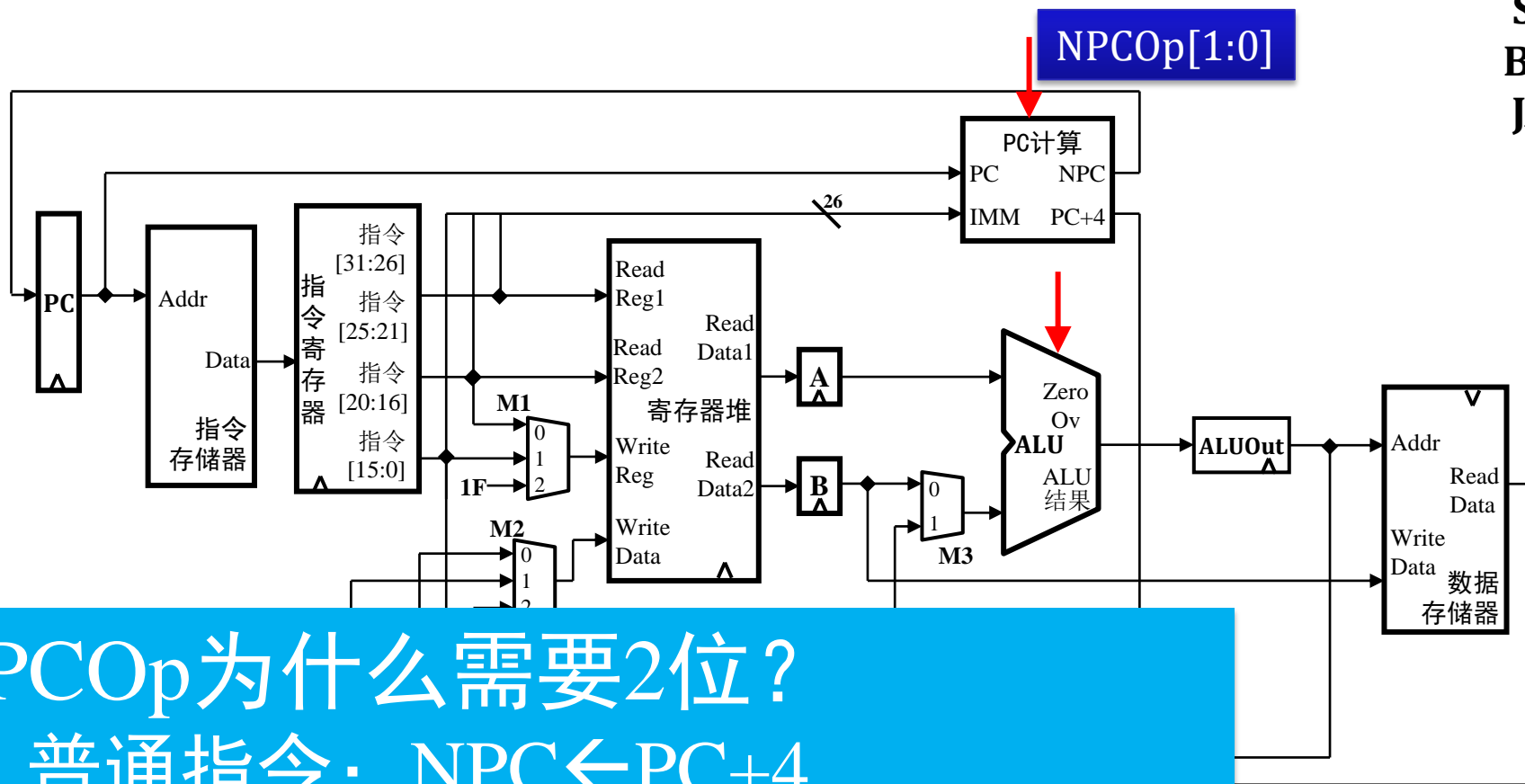
# 多周期数据通路控制信号：操作选择

LW  
ADDU  
SUBU  
ORI  
LUI  
SW  
BEQ  
JAL



NPCOp为什么需要2位？

- ◆ 普通指令：  $NPC \leftarrow PC + 4$
- ◆ BEQ：  $NPC \leftarrow PC + \text{sign\_ext}(\text{imm16})$
- ◆ JAL：  $NPC \leftarrow PC_{31..28} \parallel \text{imm26} \parallel 00$


# 多周期数据通路控制信号：操作选择

LW  
ADDU  
SUBU  
ORI  
LUI  
SW  
BEQ  
JAL

## ALUOp为什么需要2位？


01

- ◆ 无符号加、符号加、无符号减、或

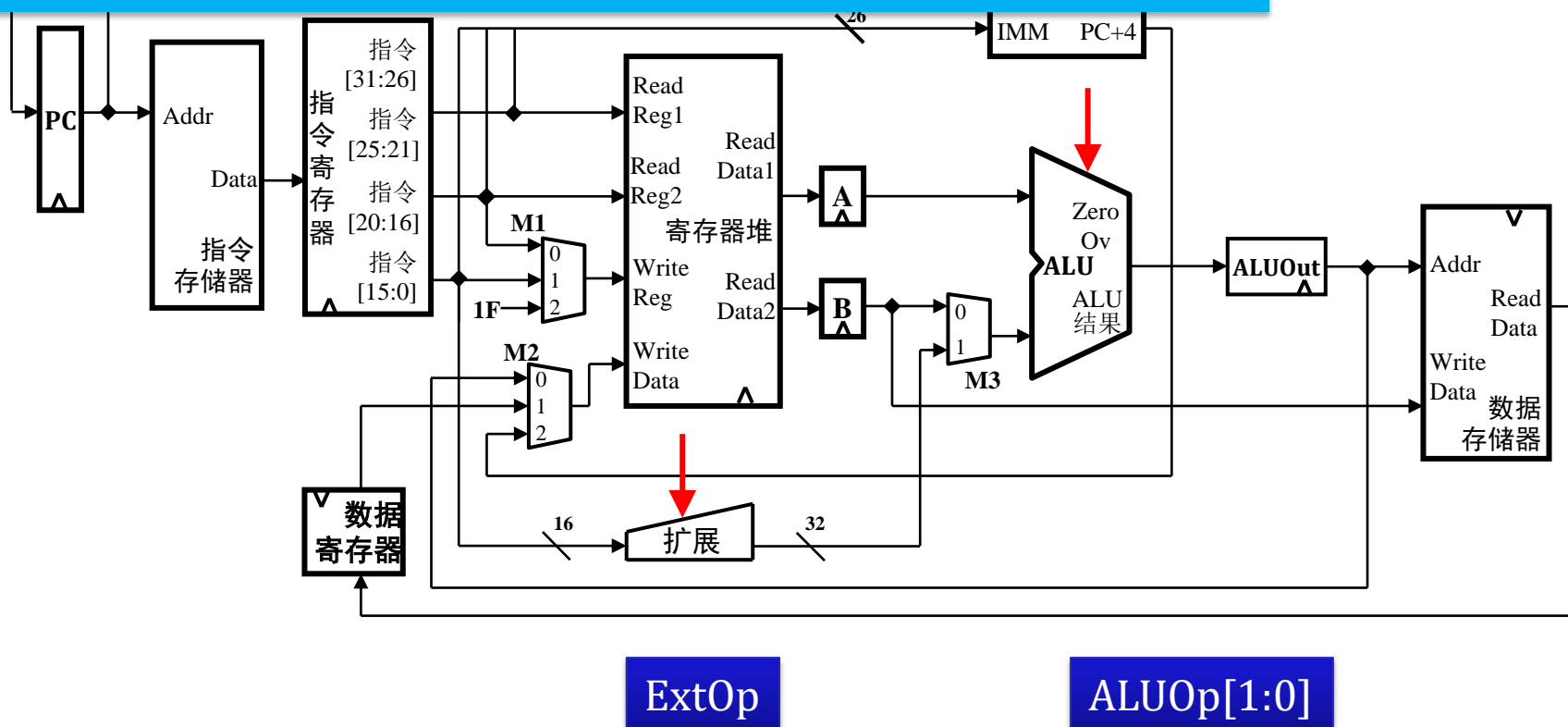

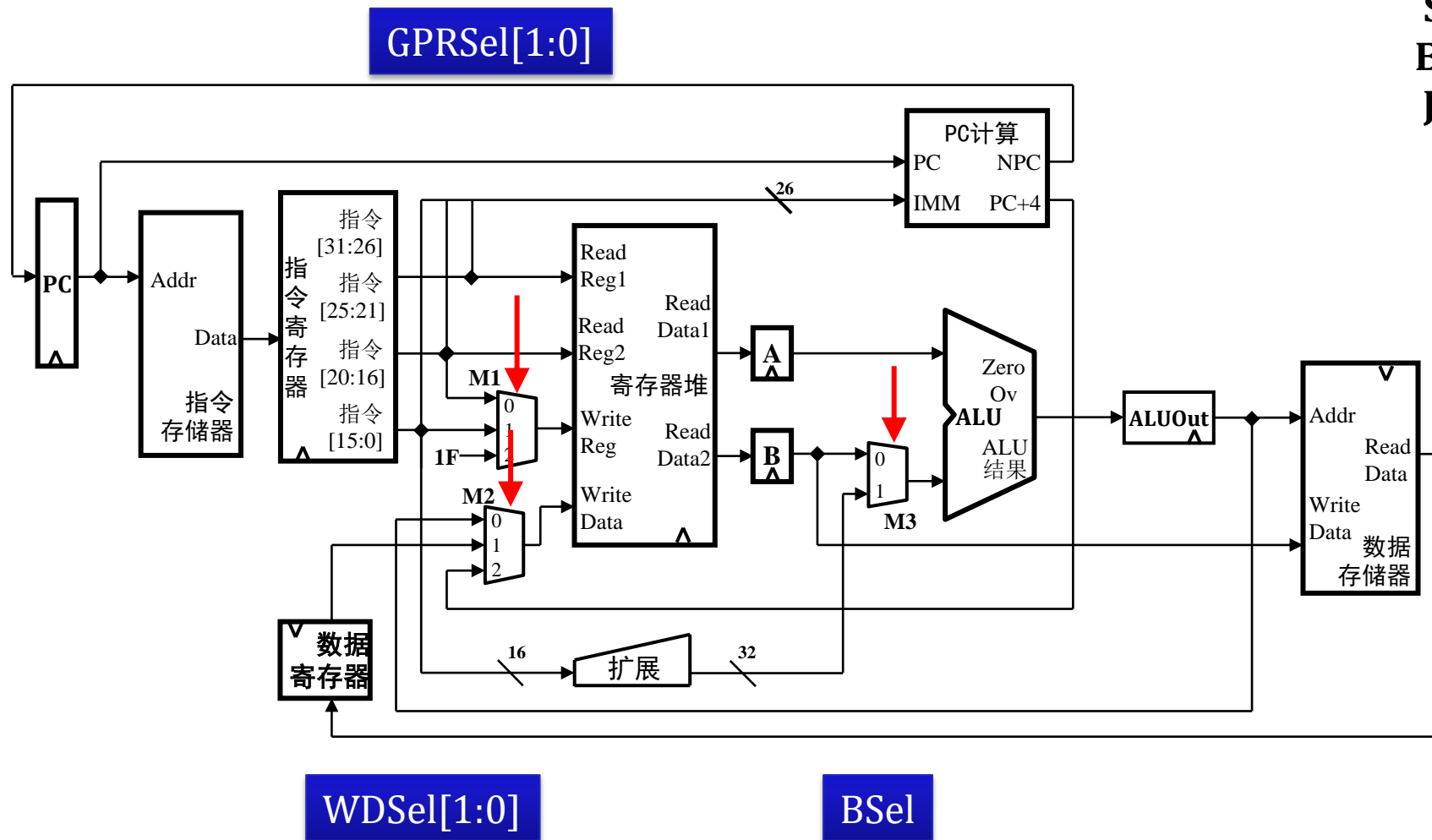
# 多周期数据通路控制信号：多路选择

LW  
ADDU  
SUBU  
ORI  
LUI  
SW  
BEQ  
JAL


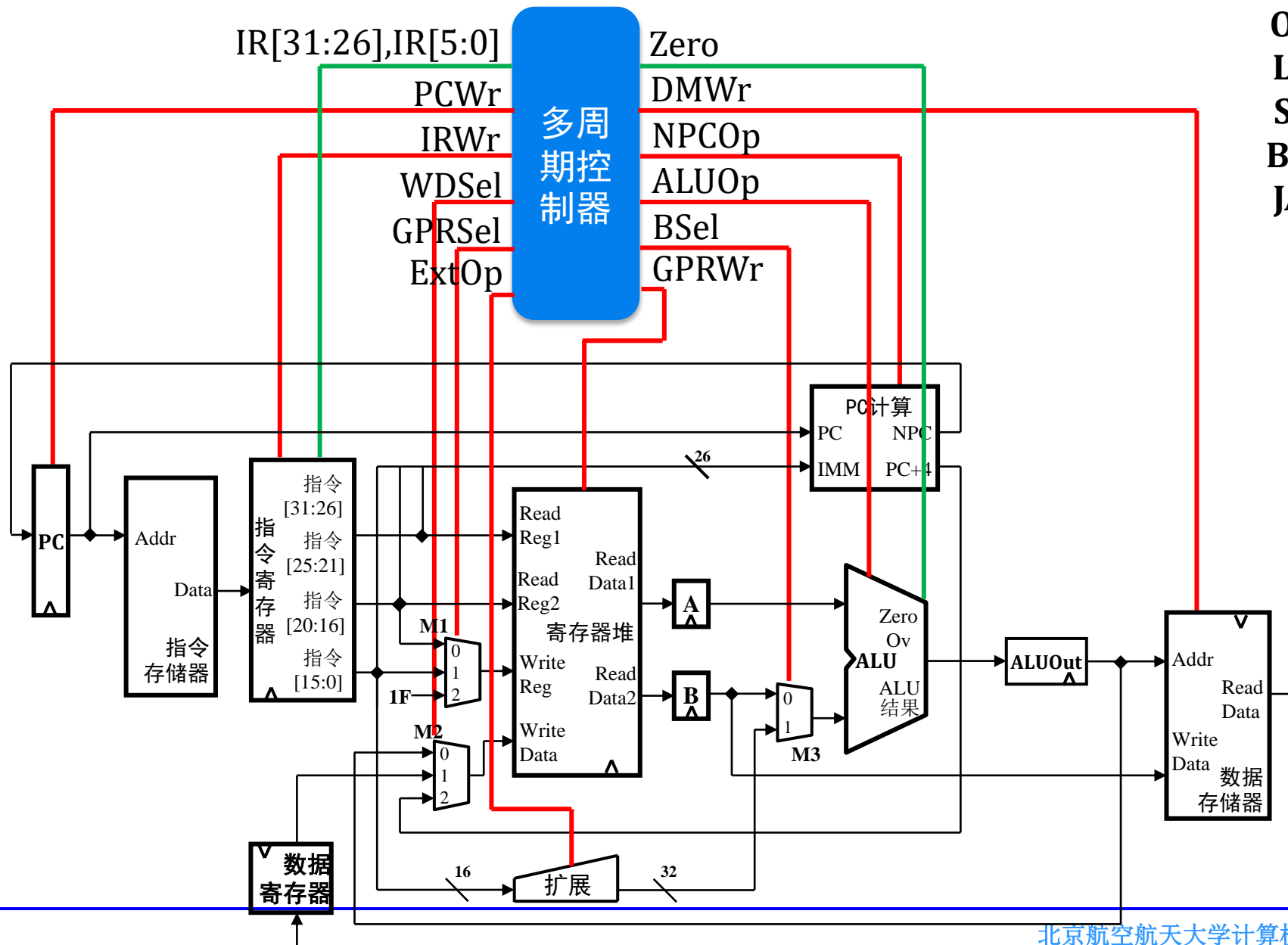
# 多周期数据通路及控制器

LW  
ADDU  
SUBU  
ORI  
LUI  
SW  
BEQ  
JAL





# 提纲


- 内容主要取材
  - 数字设计和计算机体系结构（第3章，第7章）
- 多周期数据通路控制信号分析
- 多周期控制器状态机构造
- 多周期性能分析

# 多周期控制器设计

- 数据通路：5阶段(IF、DCD/RF、EXE、MEM、WB)
  - 特点：每条指令由若3~5个时钟周期完成
- 控制器：FSM+输出逻辑
  - FSM至少应包括5个状态：分别对应数据通路的5个阶段
- FSM输入
  - Op/Funct: Instr[31:26]/Instr[5:0]
  - Zero
  - Reset, Clk
- 输出逻辑
  - 指令执行在特定阶段处于某种状态
  - Op/Funct、FSM、Zero
 
# FSM构造过程

■ **LW**, SW, ADDU, SUBU, ORI, LUI, BEQ, JAL




```
Addr ← sign_extend(offset) + GPR[base]
memword ← Memory[Addr]
GPR[rt] ← memword
PC ← PC + 4
```

RTL



$R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign\_ext}(\text{imm16})]$


$\text{PC} \leftarrow \text{PC} + 4$

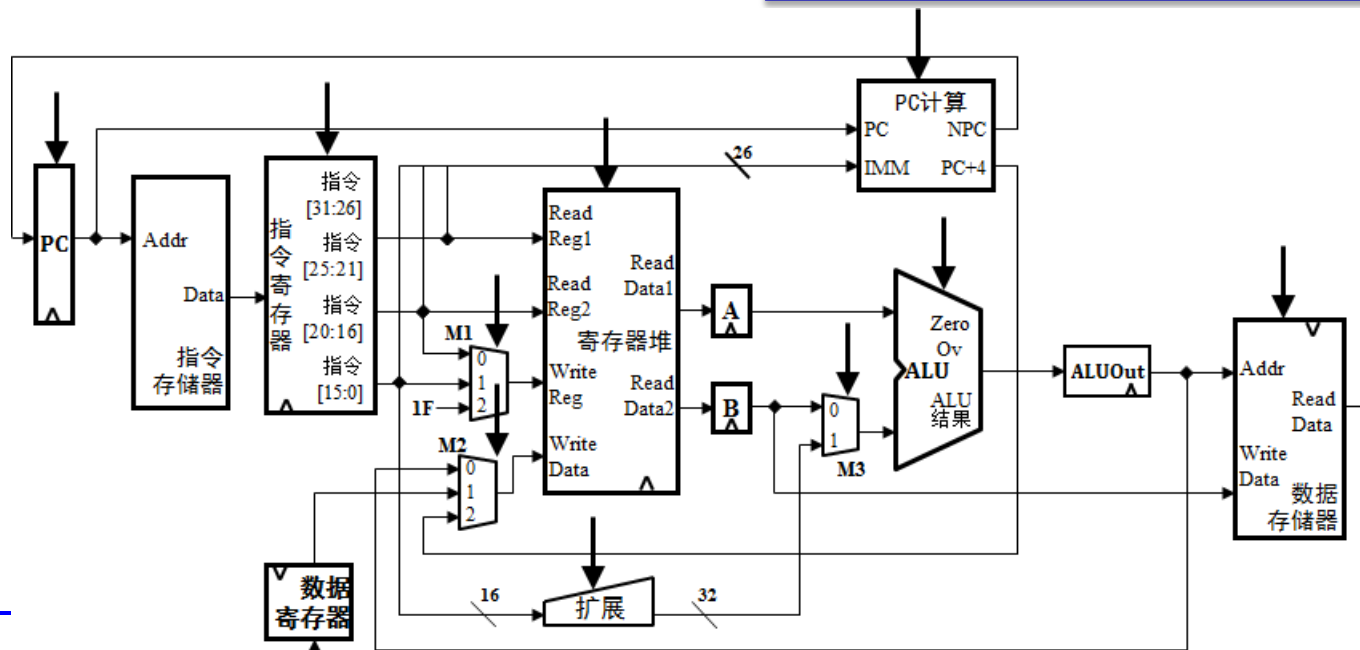






	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1									
NPCOp			PC+4									
IRWr			1									
GPRWr			0									
DMWr			0									
ALUOp			X									
GPRSel			X									
WDSel			X									
ExtOp			X									
BSel			X									

 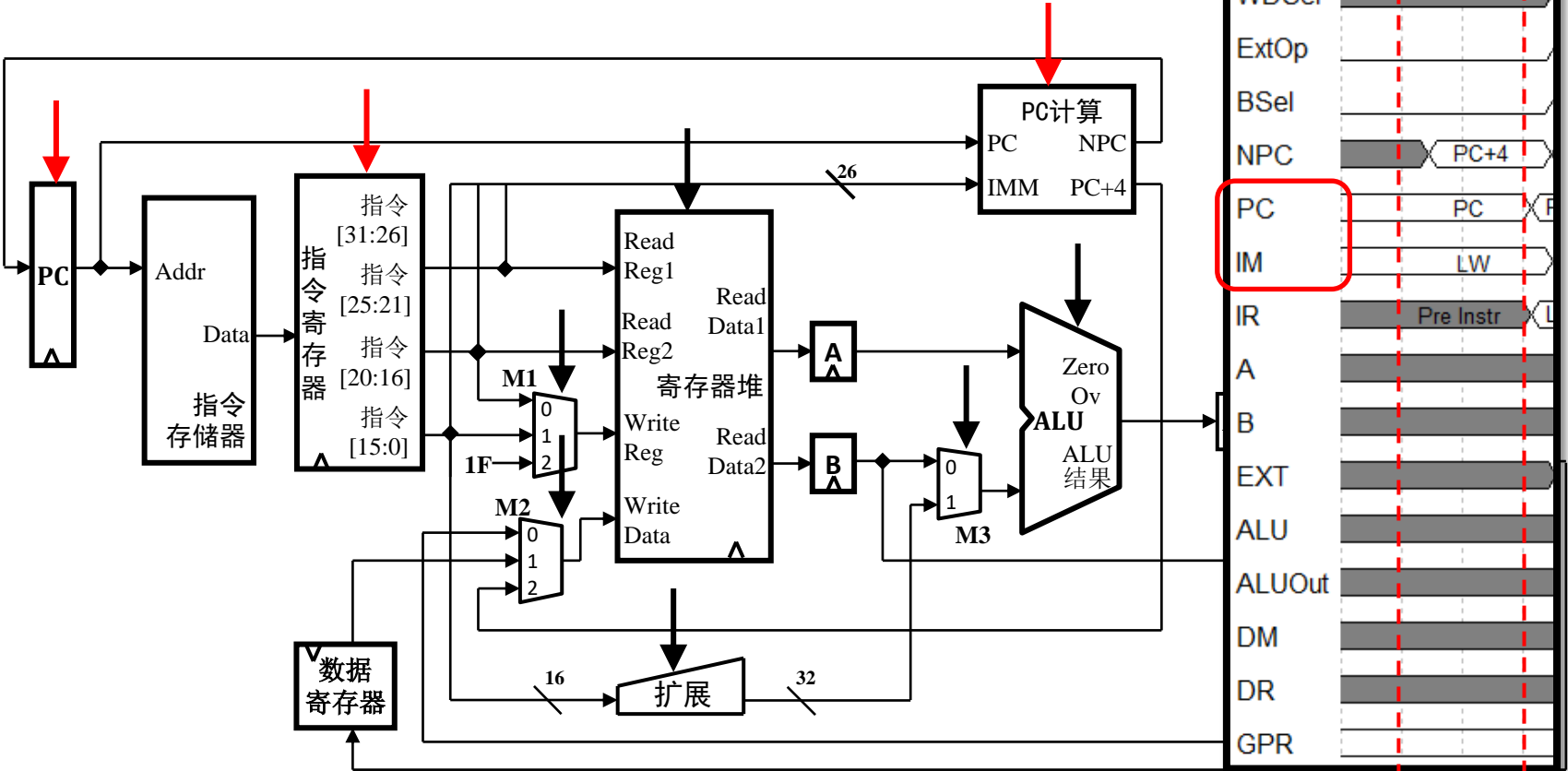

 




	Op	Funct	S0	S1	S
PCWr			1	0	
NPCOp			PC+4	X	
IRWr			1	0	
GPRWr			0	0	
DMWr			0	0	
ALUOp			X	add	
GPRSel			X	00	
WDSel			X	01	
ExtOp			X	SE	
BSel			X	1	

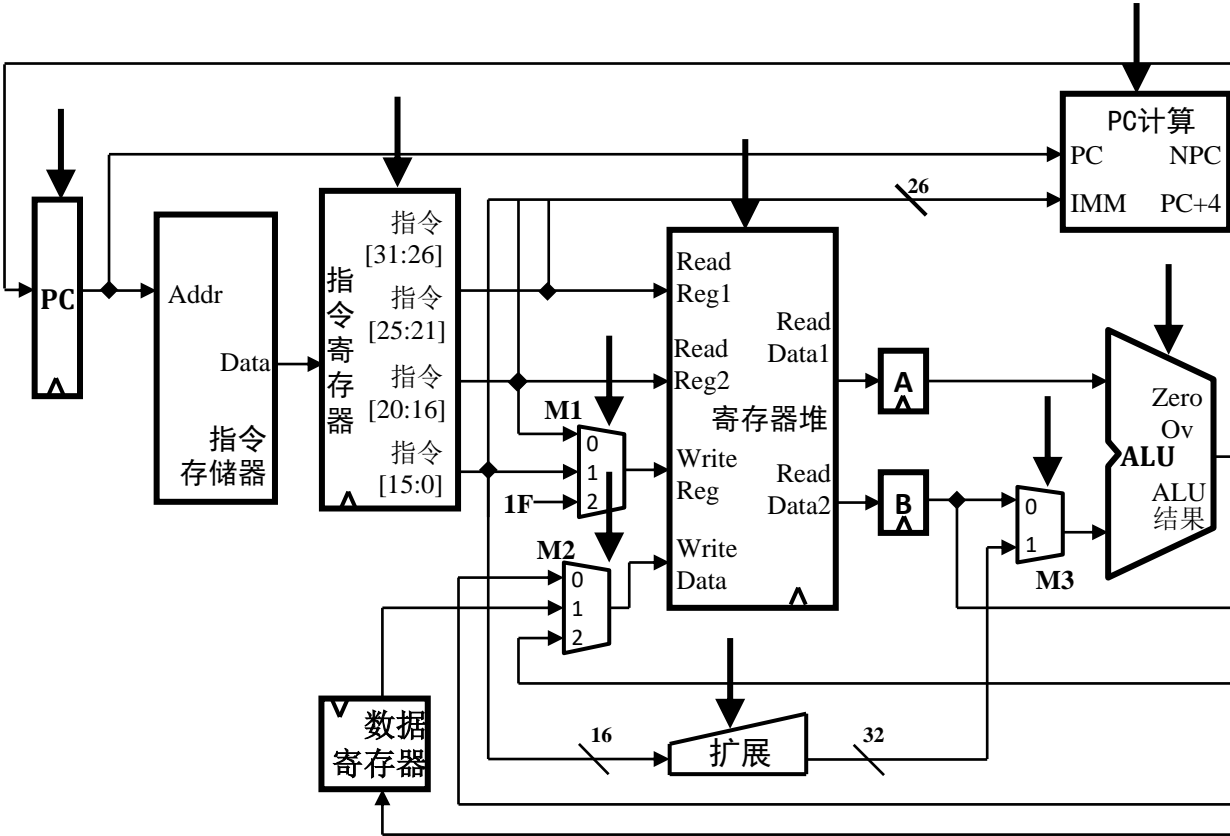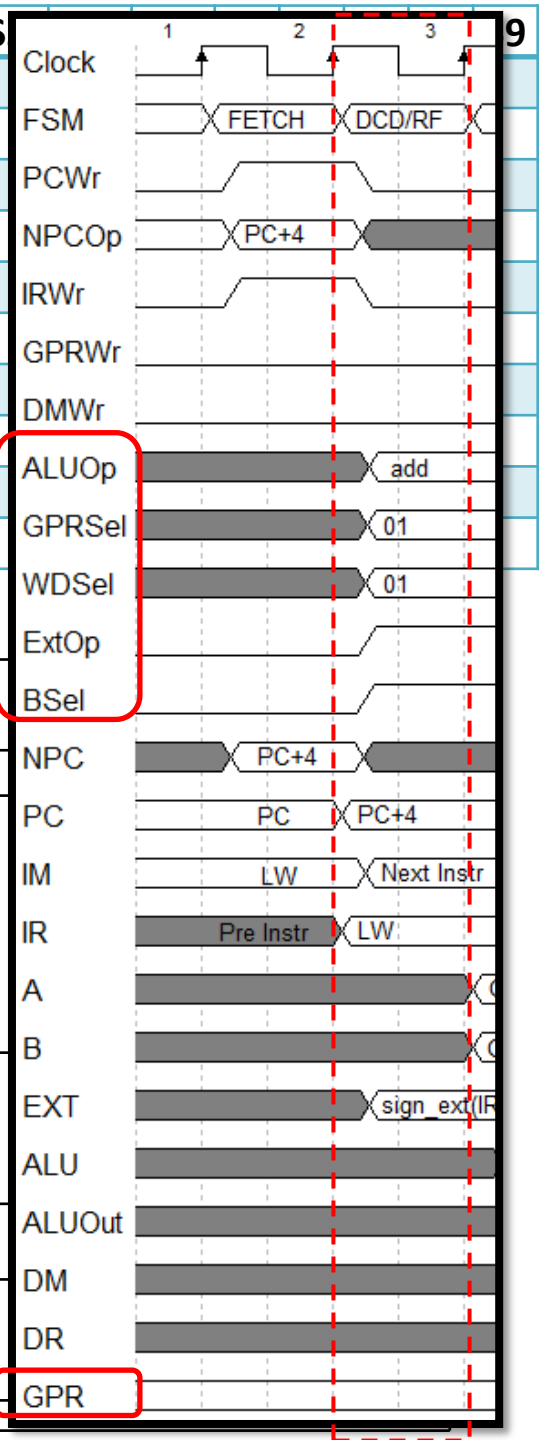

 



	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0	0							
NPCOp			PC+4	X	X							
IRWr			1	0	0							
GPRWr			0	0	0							
DMWr			0	0	0							
ALUOp			X	add	add							
GPRSel			X	00	00							
WDSel			X	01	01							
ExtOp			X	SE	SE							
BSel			X	1	1							

 

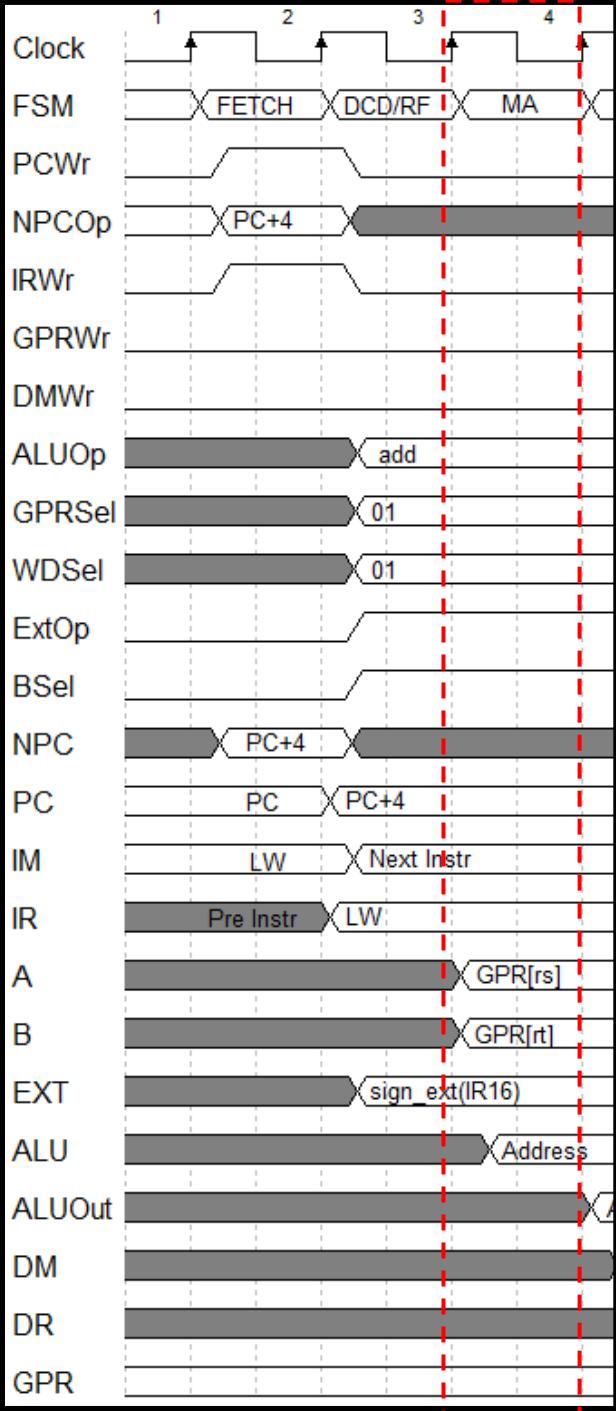 


	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
Clock	1	0	0							
FSM	1	0	0							
PCWr	1	0	0							
NPCOp	0	0	0							
IRWr	0	0	0							
GPRWr	X	add	add							
DMWr	X	00	00							
ALUOp	X	01	01							
GPRSel	X	SE	SE							
WDSel	X	1	1							

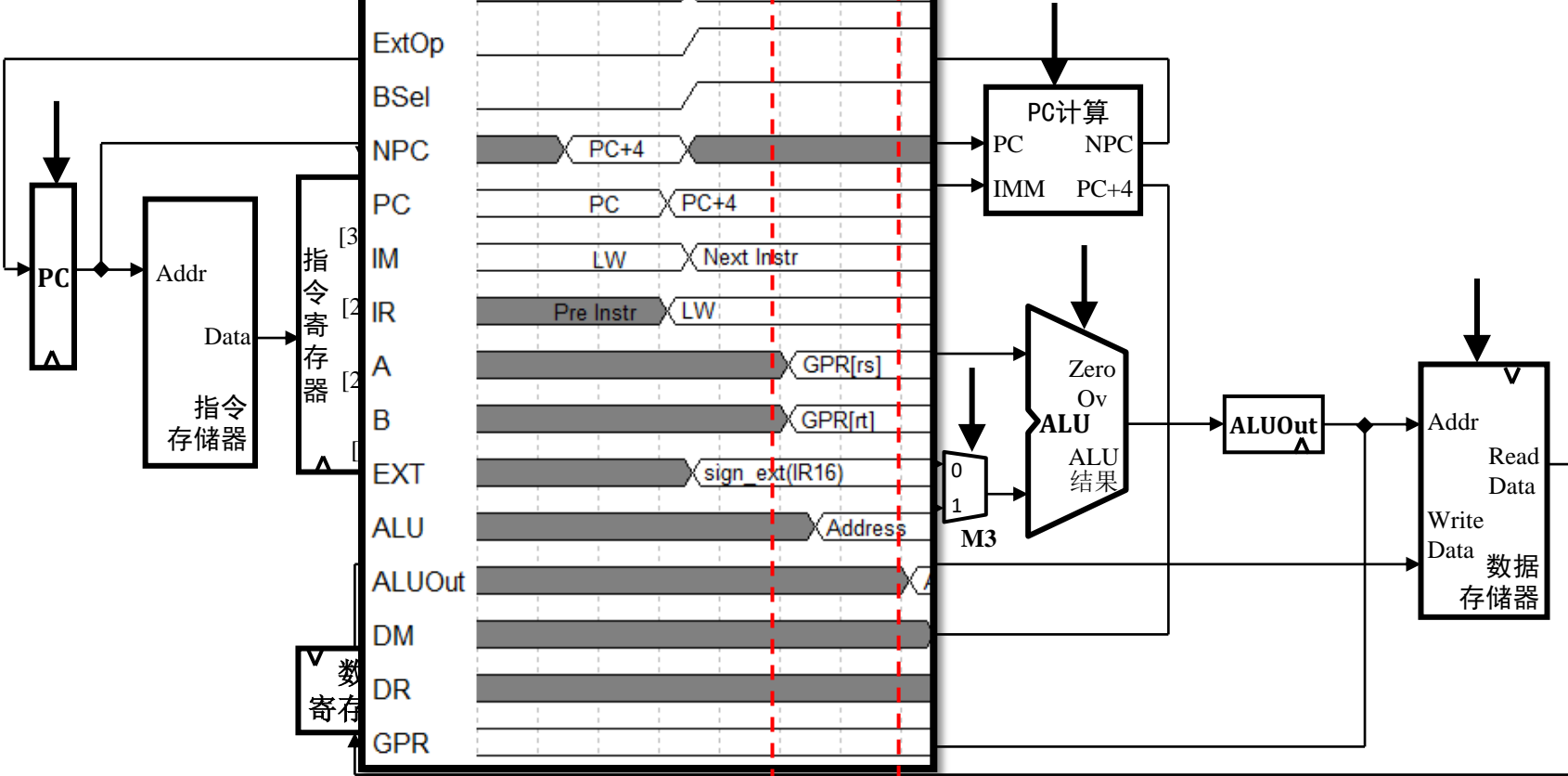


 


	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr	1	0	0	0						
NPCOp	PC+4	X	X	X						
IRWr	1	0	0	0						
GPRWr	0	0	0	0						
DMWr	0	0	0	0						
ALUOp	X	add	add	add						
GPRSel	X	00	00	00						
WDSel	X	01	01	01						
ExtOp	X	SE	SE	SE						
BSel	X	1	1	1						

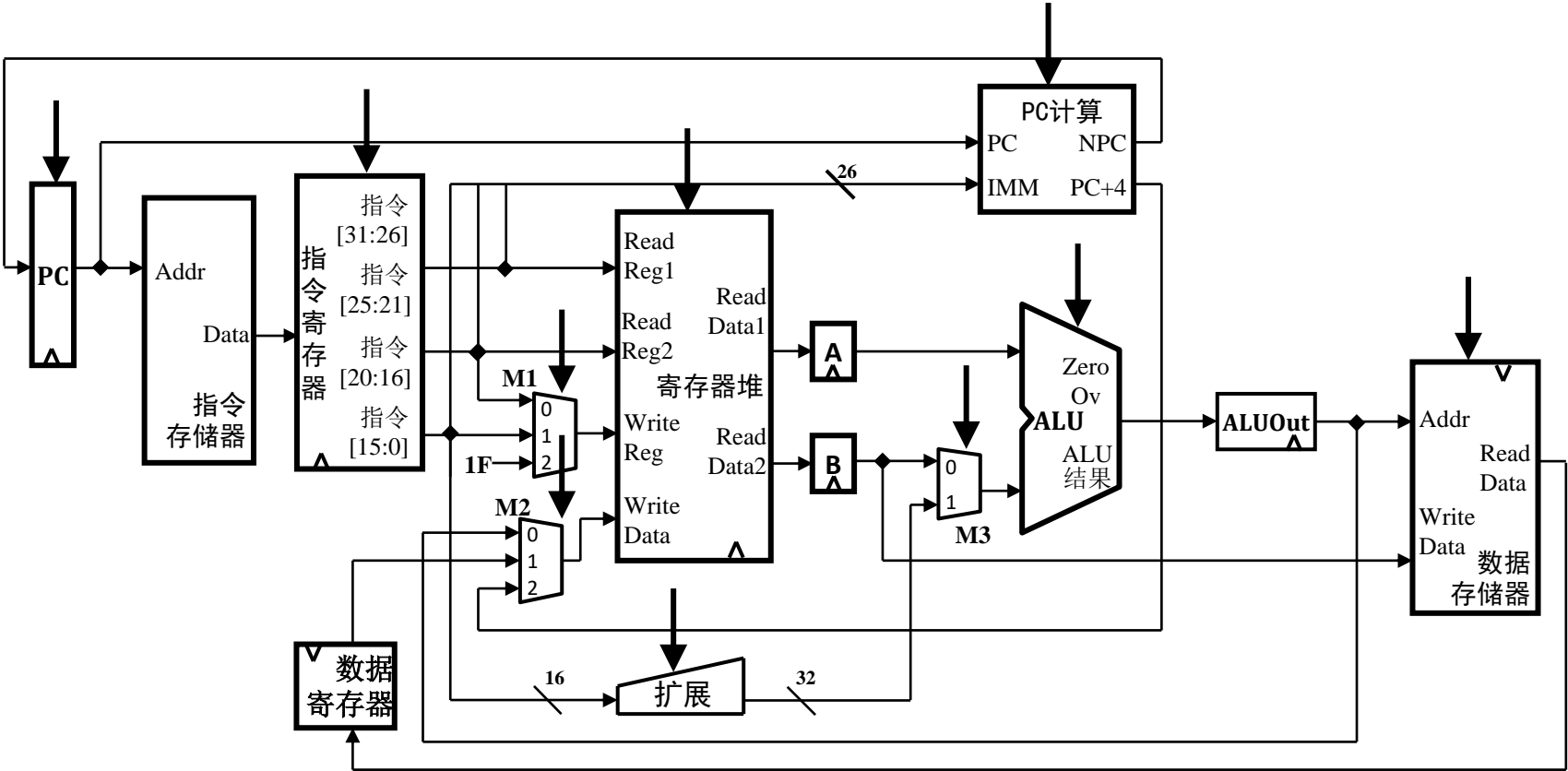






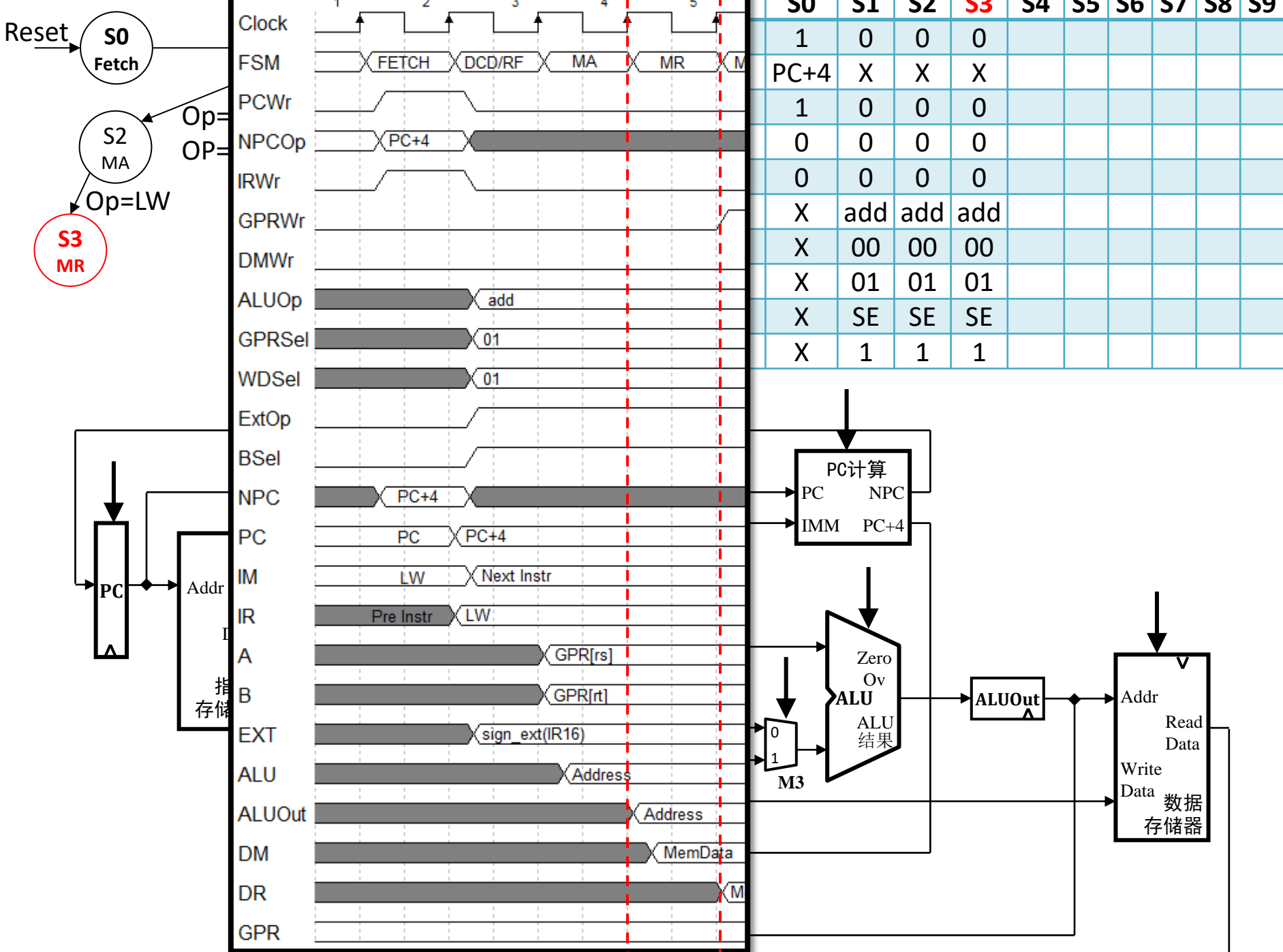


 


	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0	0	0	0					
NPCOp			PC+4	X	X	X	X					
IRWr			1	0	0	0	0					
GPRWr			0	0	0	0	1					
DMWr			0	0	0	0	0					
ALUOp			X	add	add	add	add					
GPRSel			X	00	00	00	00					
WDSel			X	01	01	01	01					
ExtOp			X	SE	SE	SE	SE					
BSel			X	1	1	1	1					

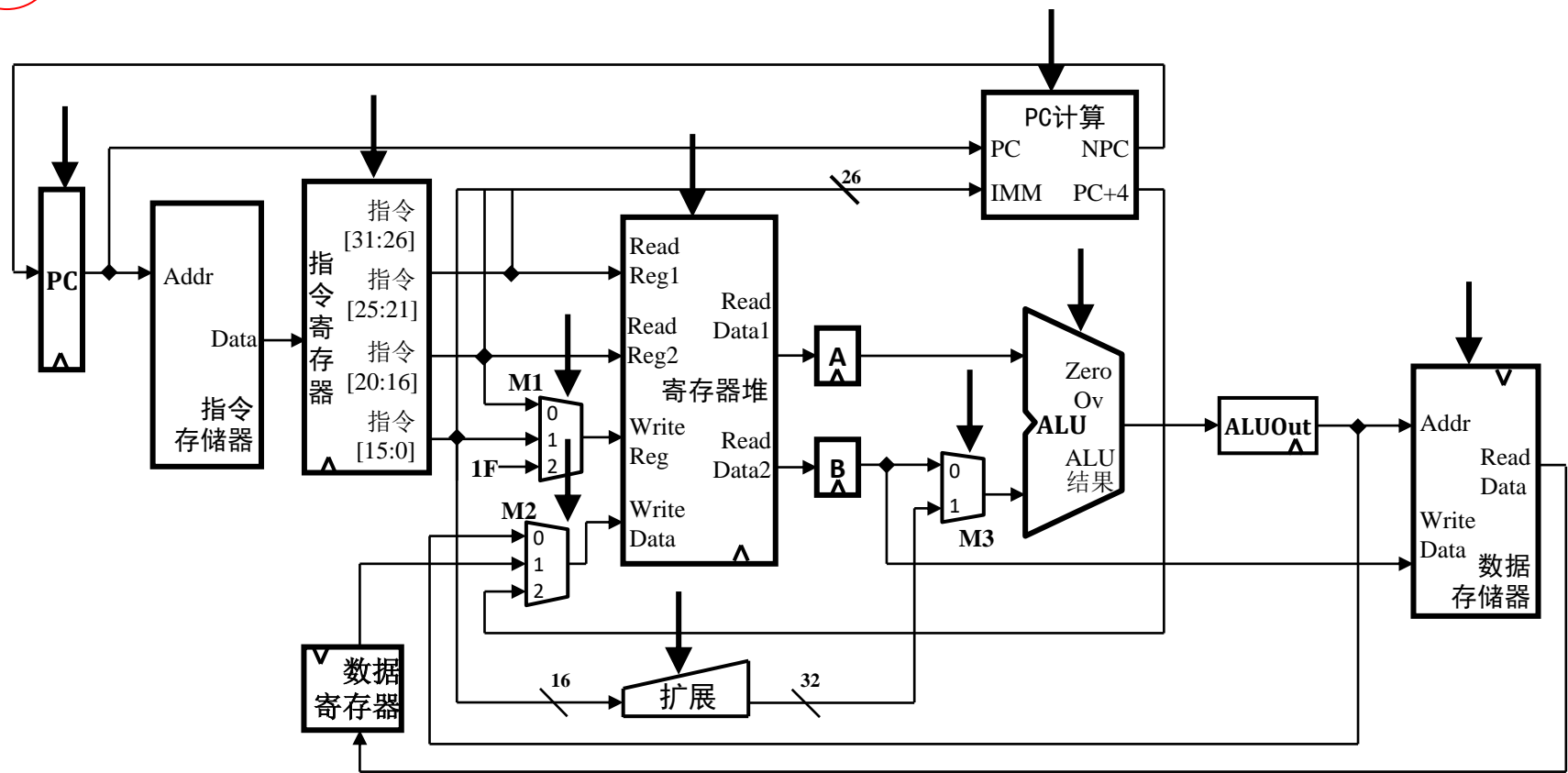

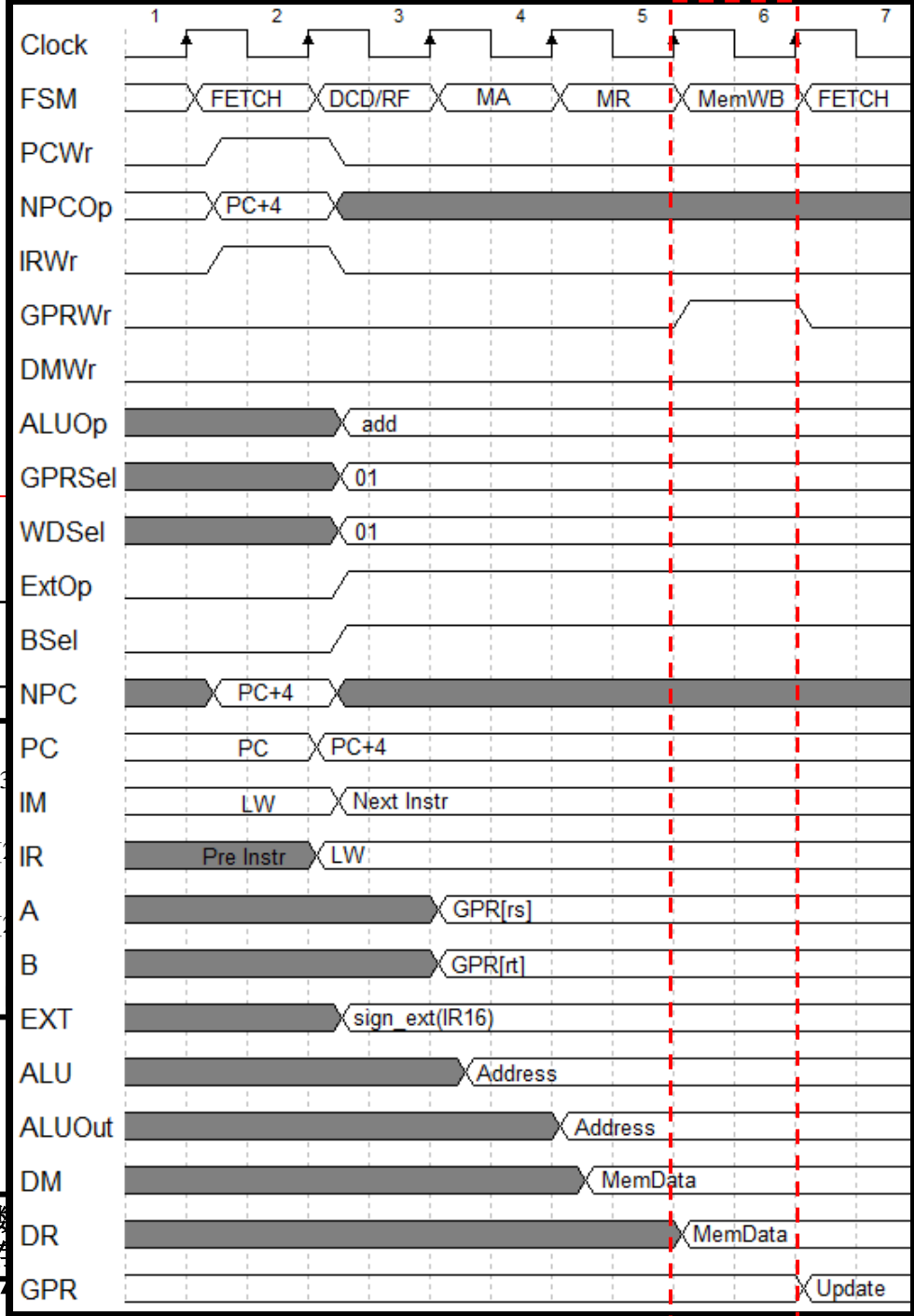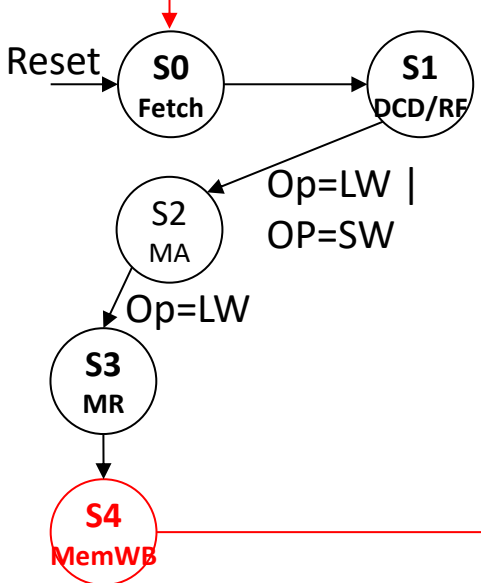


S4	S5	S6	S7	S8	S9
0					
X					
0					
1					
0					
add					
00					
01					
SE					
1					

 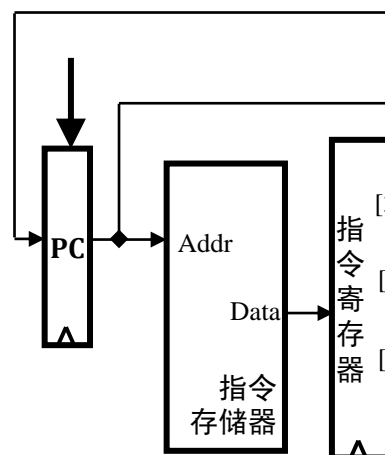
 
# FSM构造过程

■ LW, **SW**, ADDU, SUBU, ORI, LUI, BEQ, JAL





$\text{Addr} \leftarrow \text{sign\_extend}(\text{offset}) + \text{GPR}[\text{base}]$   
 $\text{memword} \leftarrow \text{Memory}[\text{Addr}]$   
 $\text{GPR}[\text{rt}] \leftarrow \text{memword}$   
 $\text{PC} \leftarrow \text{PC} + 4$

RTL描述


$\text{MEM}[\text{R}[\text{rs}] + \text{sign\_ext}(\text{imm16})] \leftarrow \text{R}[\text{rt}]$

$\text{PC} \leftarrow \text{PC} + 4$

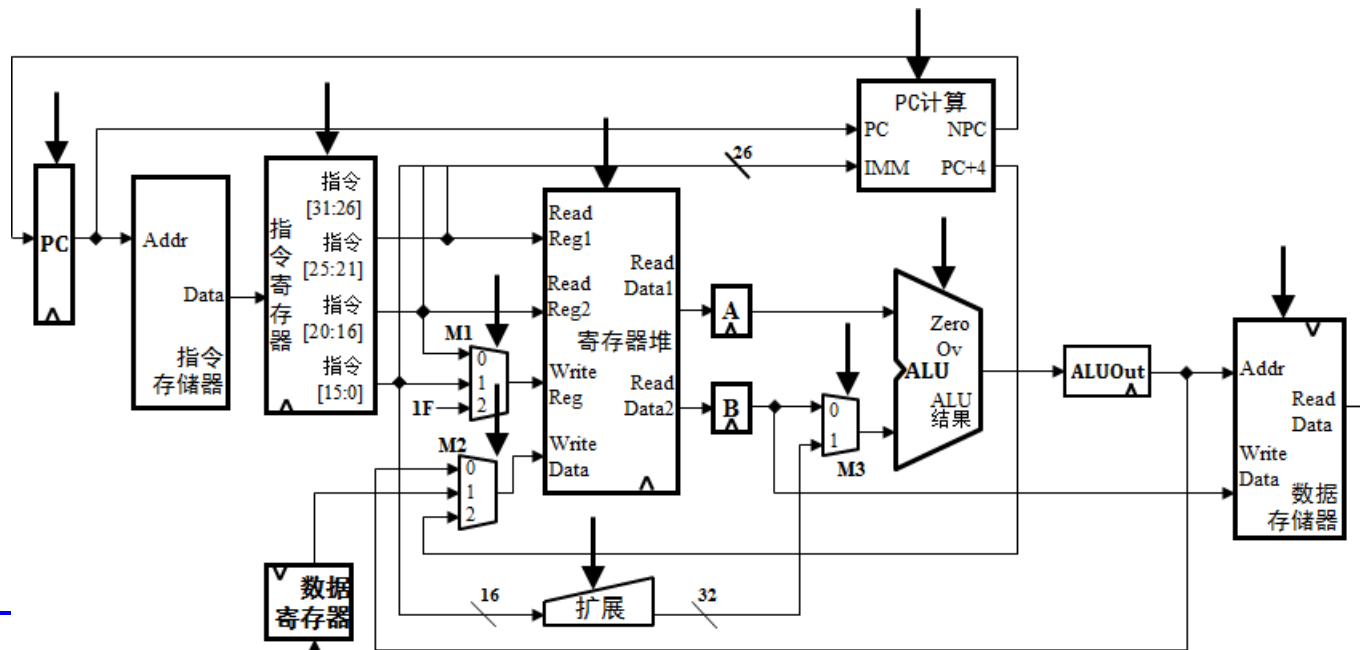

 


	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0	0		0					
NPCOp			PC+4	X	X		X					
IRWr			1	0	0		0					
GPRWr			0	0	0		0					
DMWr			0	0	0		1					
ALUOp			X	add	add		add					
GPRSel			X	00	00		00					
WDSel			X	01	01		01					
ExtOp			X	SE	SE		SE					
BSel			X	1	1		1					

 
 
# FSM构造过程

■ LW, SW, **ADDU**, SUBU, ORI, LUI, BEQ, JAL




Operation:


```
temp ← GPR[rs] + GPR[rt]
GPR[rd] ← temp
```

RTL


$R[rd] \leftarrow R[rs] + R[rt]$

$PC \leftarrow PC + 4$

 

 

	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0					0			
NPCOp			PC+4	X					X			
IRWr			1	0					0			
GPRWr			0	0					0			
DMWr			0	0					0			
ALUOp			X	add					add			
GPRSel			X	01					01			
WDSel			X	00					00			
ExtOp			X	X					X			
BSel			X	0					0			

 





 
# FSM构造过程

- LW, SW, ADDU, SUBU, **ORI**, LUI, BEQ, JAL




Operation:


$GPR[rt] \leftarrow GPR[rs] \text{ or } \text{zero\_extend}(\text{imm16})$

RTL


$R[rd] \leftarrow R[rs] \mid \text{zero\_extend}(\text{imm16})$


$PC \leftarrow PC + 4$

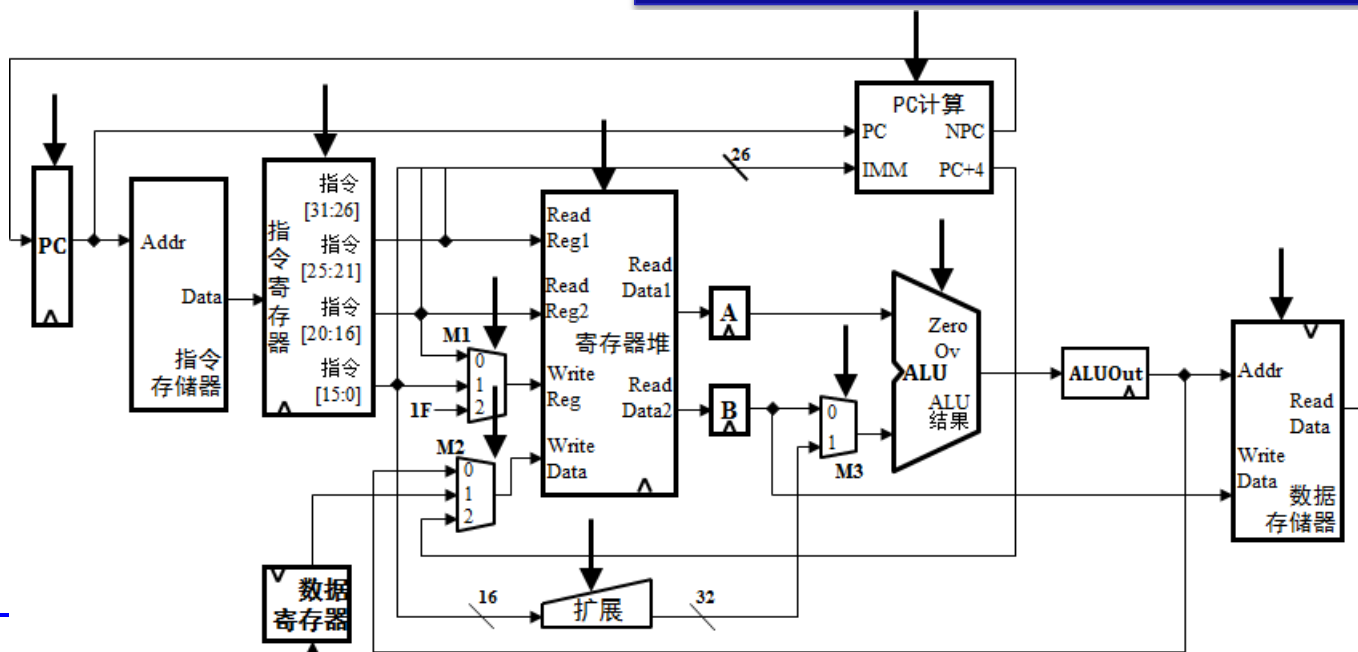

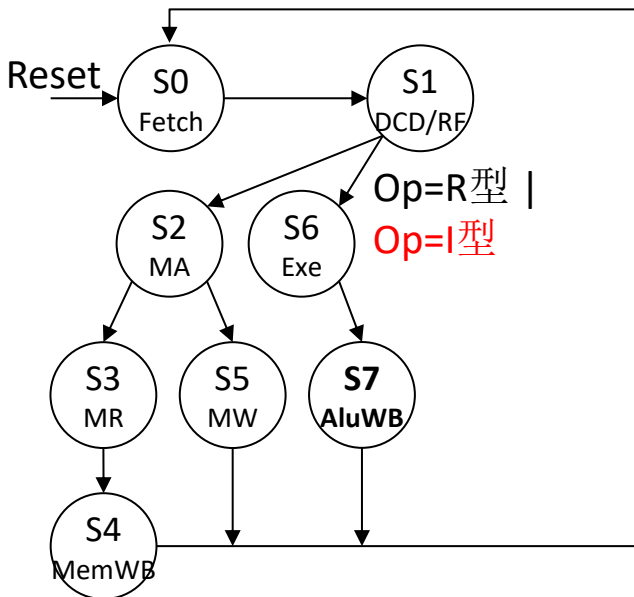

	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0					0	0		
NPCOp			PC+4	X					X	X		
IRWr			1	0					0	0		
GPRWr			0	0					0	1		
DMWr			0	0					0	0		
ALUOp			X	OR					OR	OR		
GPRSel			X	00					00	00		
WDSel			X	00					00	00		
ExtOp			X	ZE					ZE	ZE		
BSel			X	1					1	1		

 


 

	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0					0	0		
NPCOp			PC+4	X					X	X		
IRWr			1	0					0	0		
GPRWr			0	0					0	1		
DMWr			0	0					0	0		
ALUOp			X	OR					OR	OR		
GPRSel			X	00					00	00		
WDSel			X	00					00	00		
ExtOp			X	ZE					ZE	ZE		
BSel			X	1					1	1		

I型与R型没有实质差别！区别仅在于：



- ALU的B通道的控制

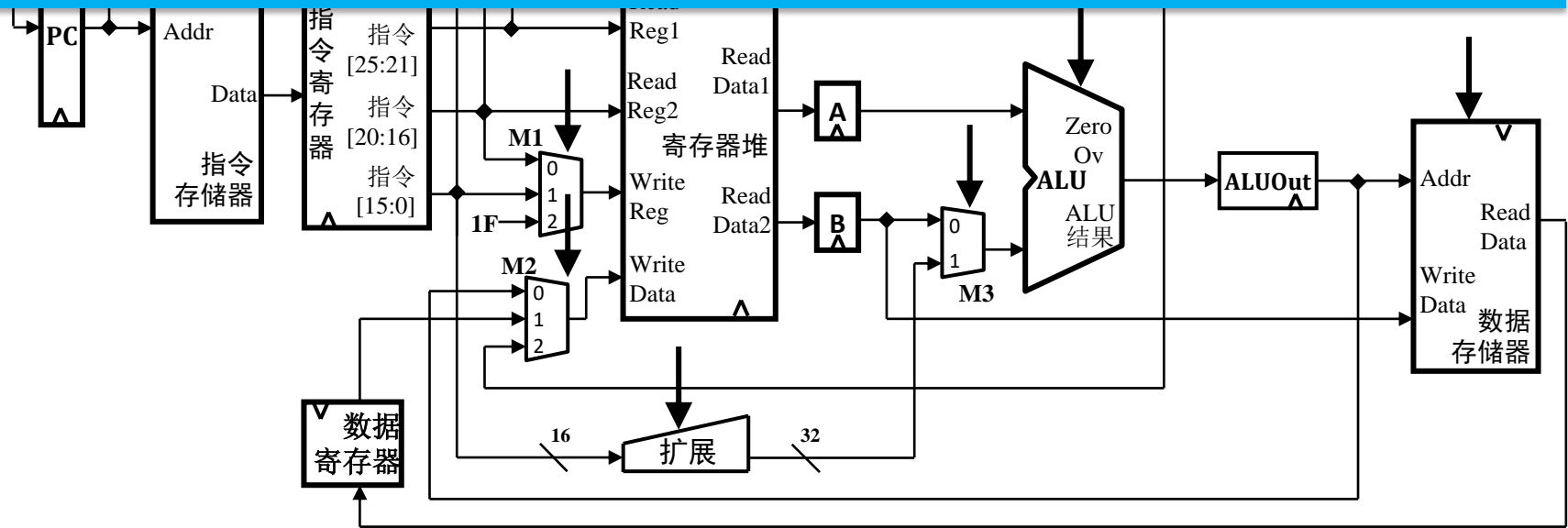

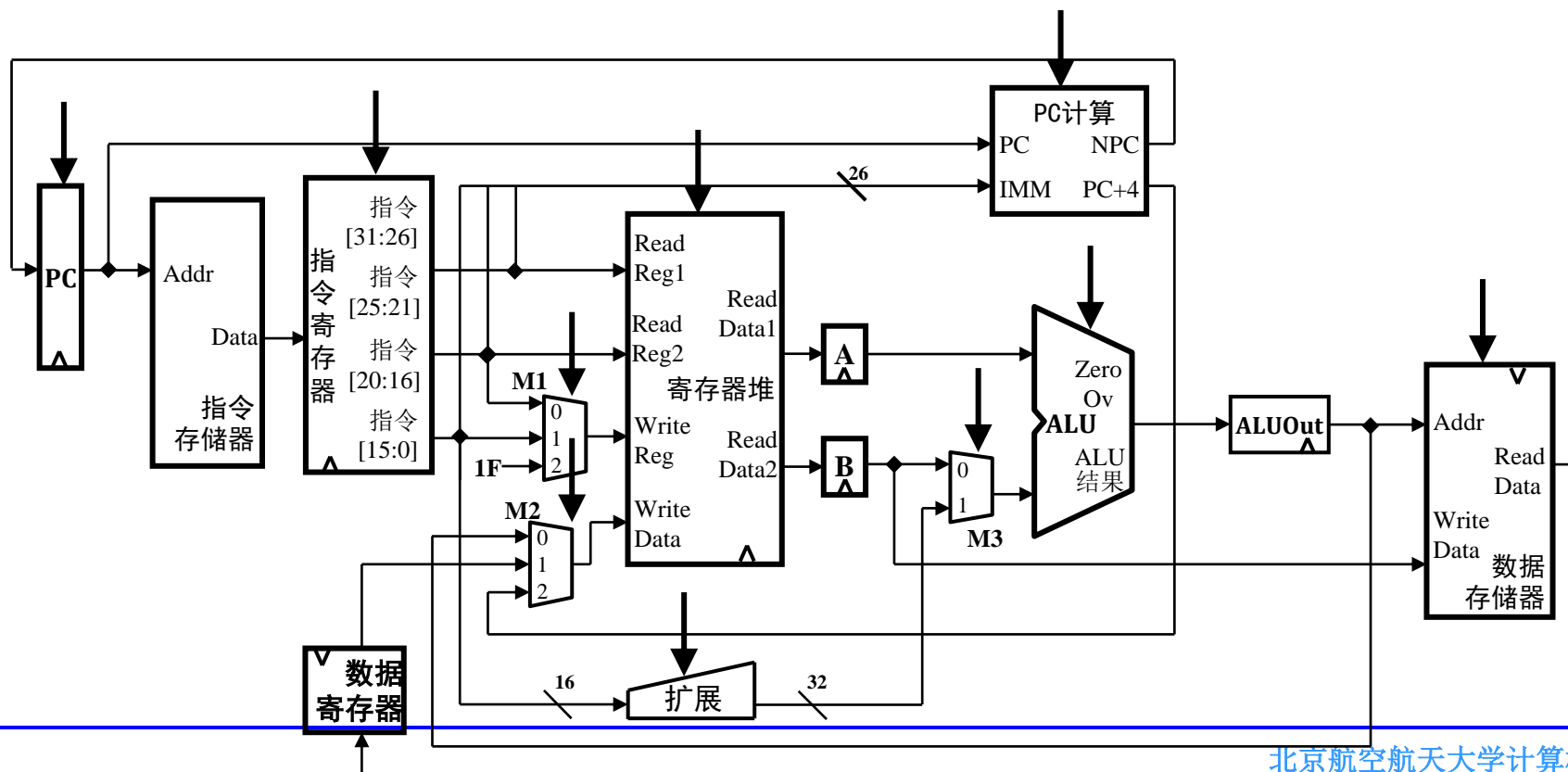 
# FSM构造过程


- LW, SW, ADDU, SUBU, ORI, LUI, BEQ, JAL
- LUI怎么执行?

□  $GPR[rt] \leftarrow imm16 \parallel 0^{16}$



 

	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0								
NPCOp			PC+4	X								
IRWr			1	0								
GPRWr			0	0								
DMWr			0	0								
ALUOp			X									
GPRSel			X	00								
WDSel			X	00								
ExtOp			X									
BSel			X	1								

 





# FSM构造过程


- LW, SW, ADDU, SUBU, ORI, LUI, **BEQ**, JAL

```
beq    if (R[rs]==R[rt])  
       then PC←PC+4+[sign_ext(imm16)||00]  
       else PC←PC+4
```

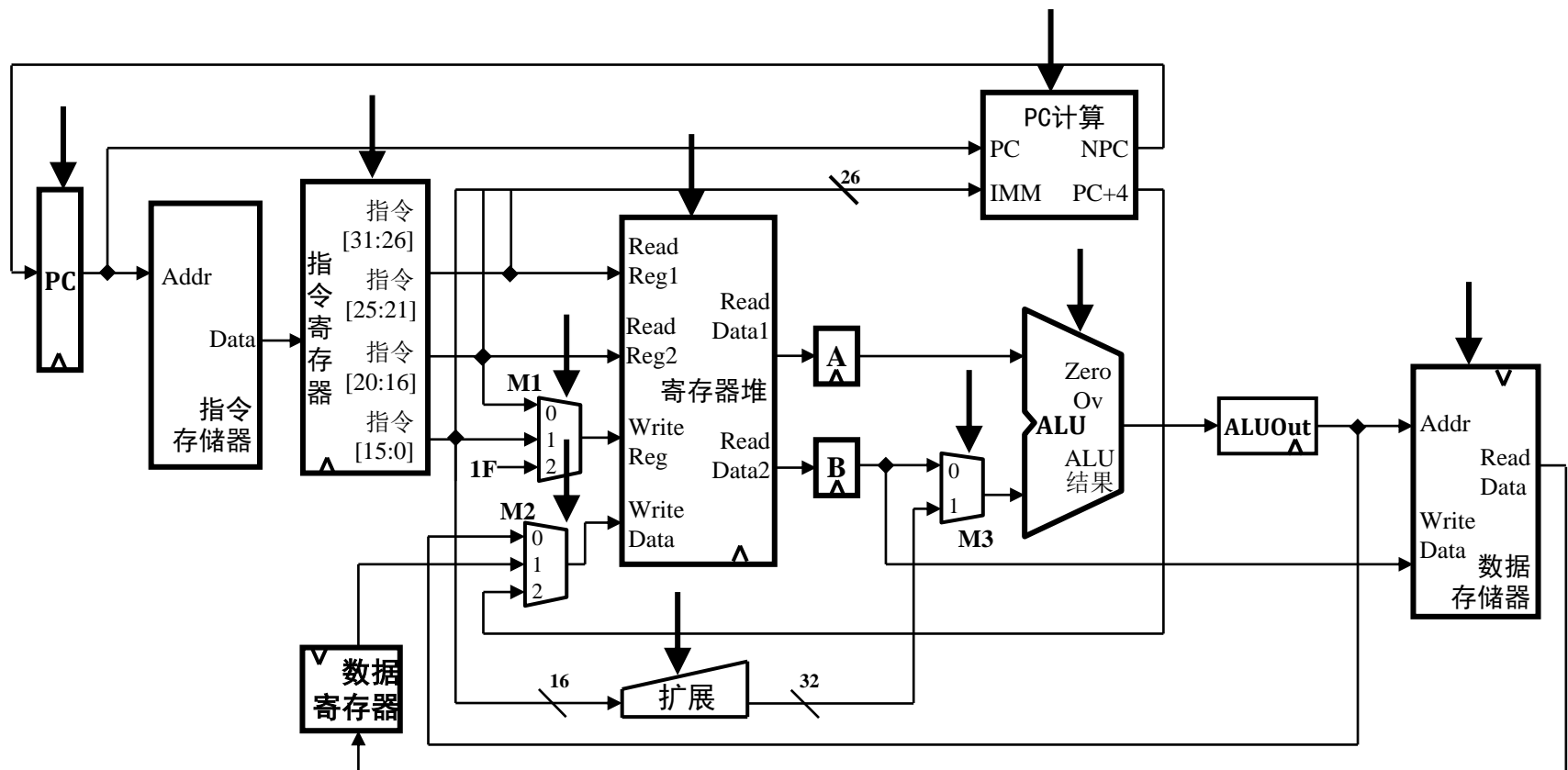


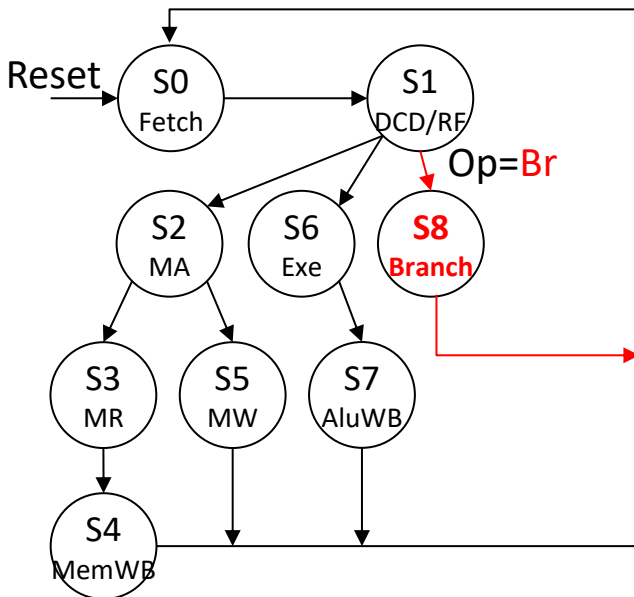



	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0							0/1	
NPCOp			PC+4	BEQ								
IRWr			1	0								
GPRWr			0	0								
DMWr			0	0								
ALUOp			X	SUB							SUB	
GPRSel			X	X							X	
WDSel			X	X							X	
ExtOp			X	X							X	
BSel			X	0							0	

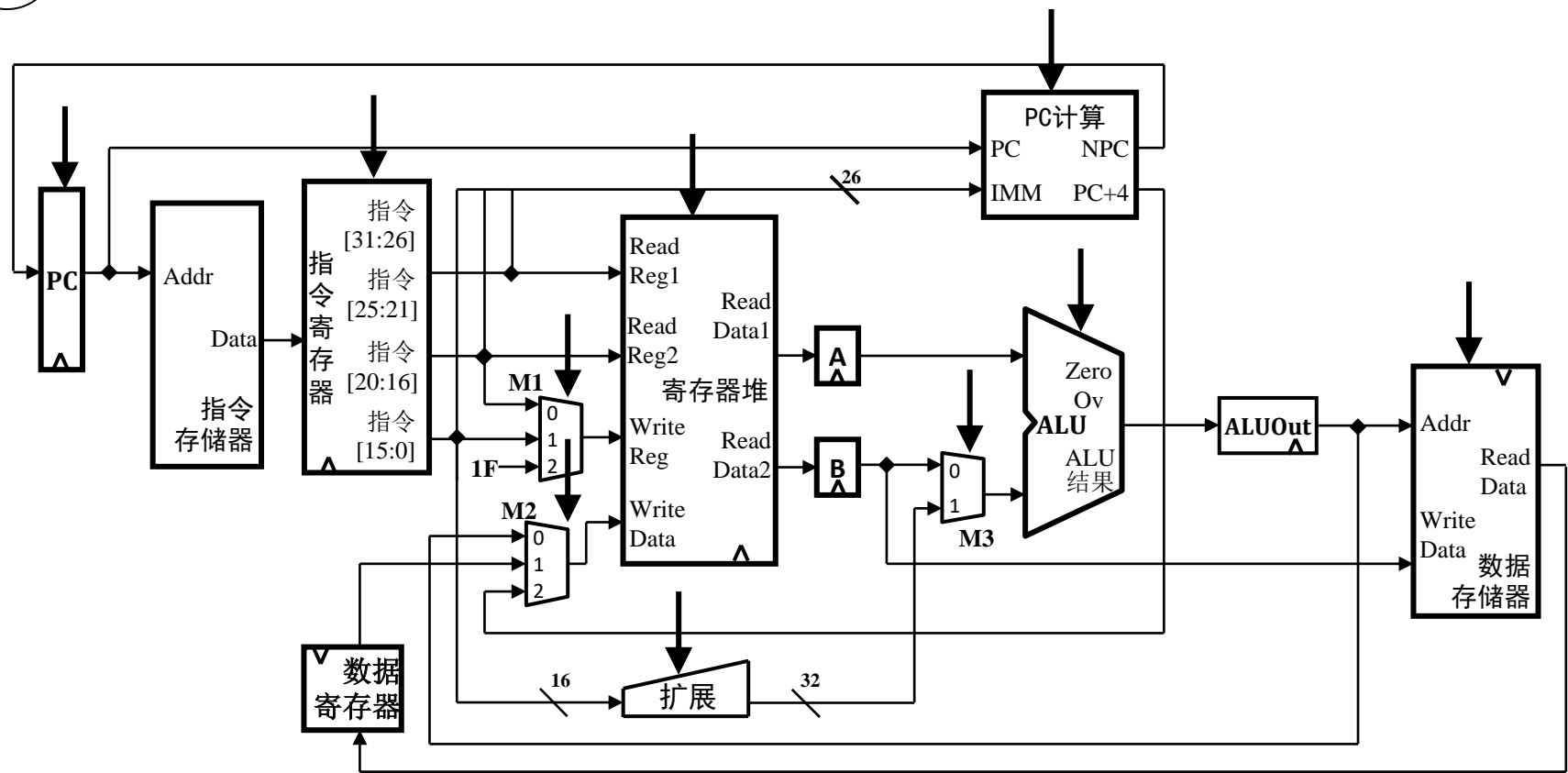




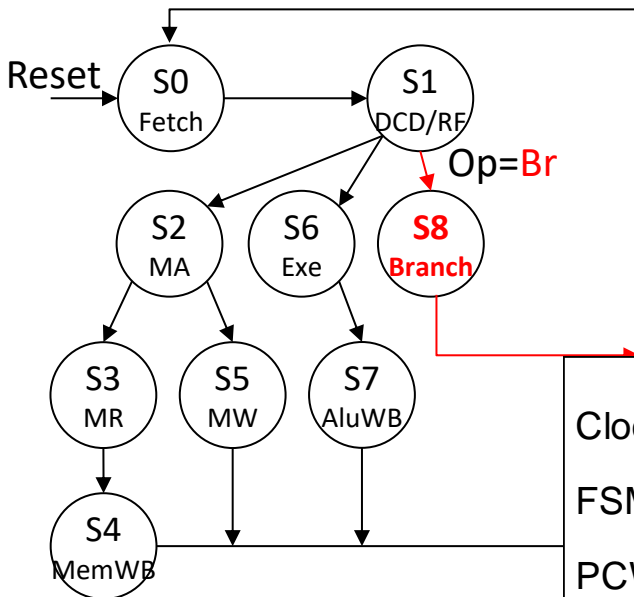

	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0							0/1	
NPCOp			PC+4	BEQ								
IRWr			1	0								
GPRWr			0	0								
DMWr			0	0								
ALUOp			X	SUB							SUB	

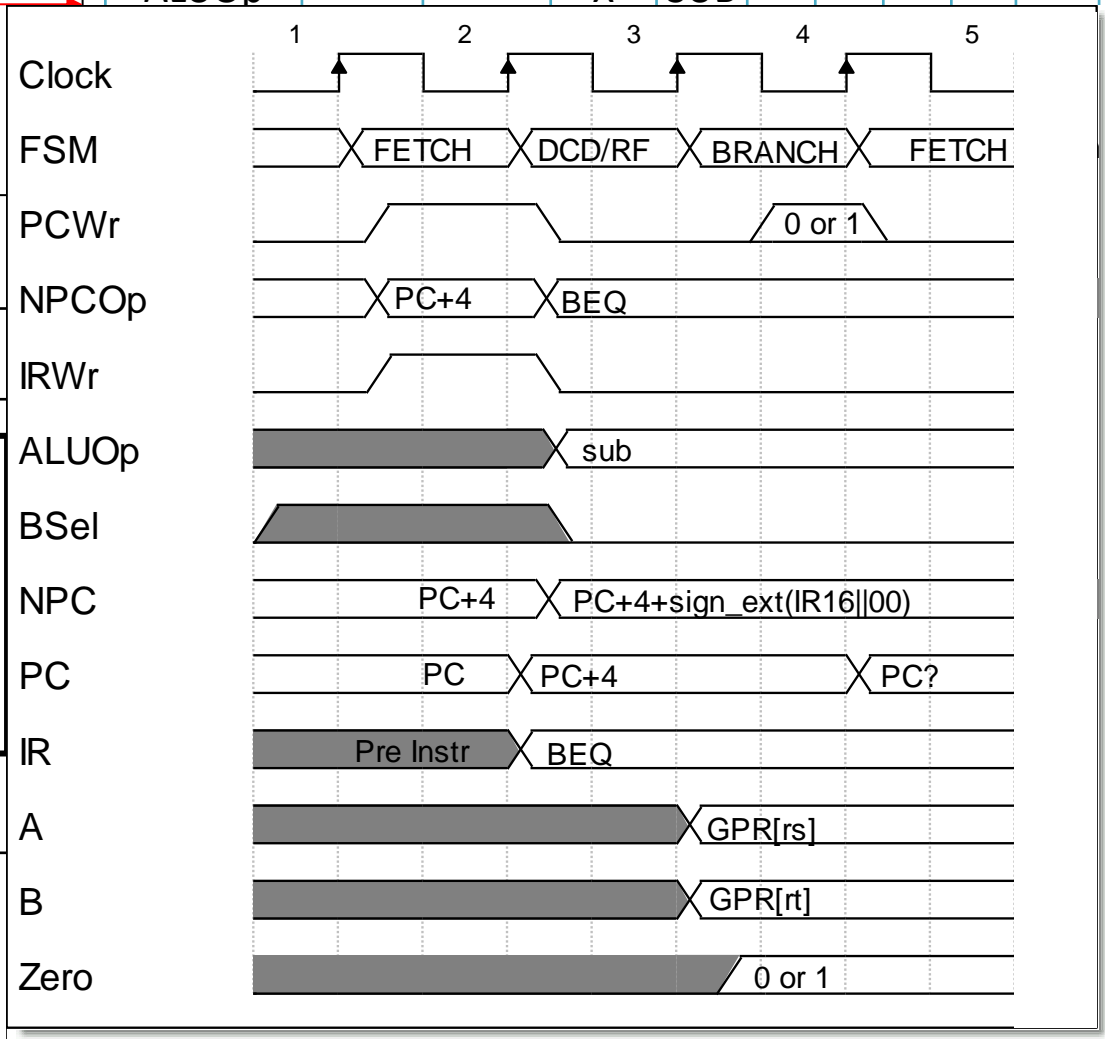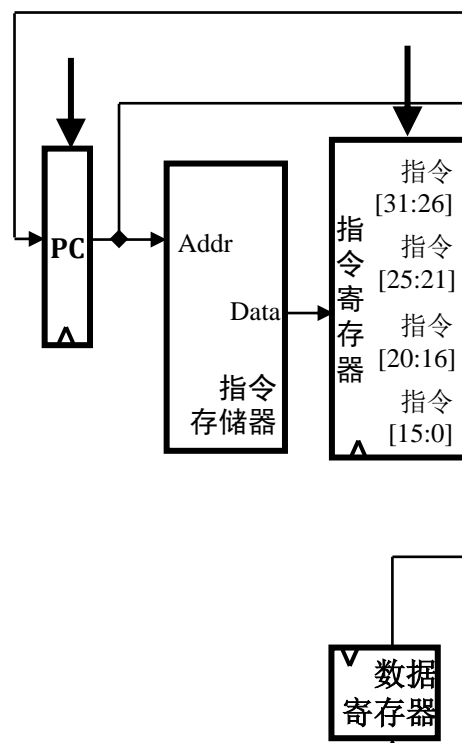

	X	
	X	
	X	
	0	

 



# FSM构造过程

- LW, SW, ADDU, SUBU, ORI, LUI, BEQ, **JAL**


**I:**  $\text{GPR}[31] \leftarrow \text{PC} + 8$

 **I+1:**  $\text{PC} \leftarrow \text{PC}_{\text{GPRLEN}-1..28} \parallel \text{instr\_index} \parallel 0^2$



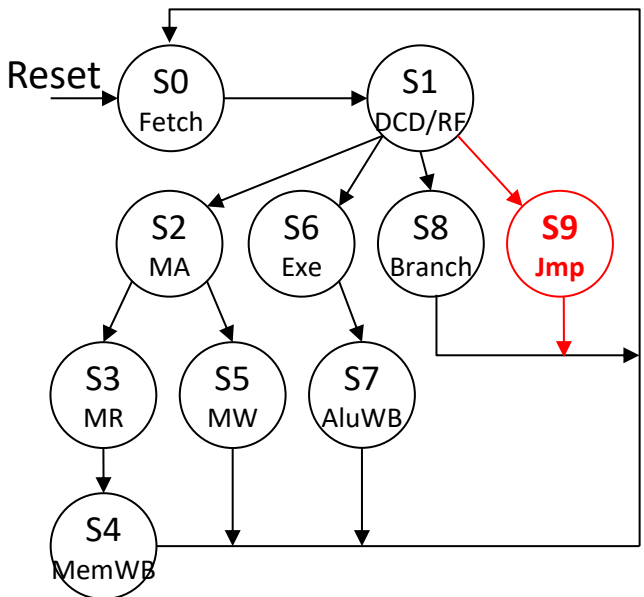

	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr			1	0								1
NPCOp			PC+4	BEQ								JAL
IRWr			1	0								0
GPRWr			0	0								1
DMWr			0	0								0
ALUOp			X	X								X
GPRSel			X	10								10
WDSel			X	10								10
ExtOp			X	X								X
BSel			X	X								X

 

# 综合信号：第1步

- 用变量表达所有指令

$\text{beq} = \text{op}[5]' \cdot \text{op}[4]' \cdot \text{op}[3]' \cdot \text{op}[2] \cdot \text{op}[1]' \cdot \text{op}[0]'$

。 。 。

$\text{Rtype} = \text{op}[5]' \cdot \text{op}[4]' \cdot \text{op}[3]' \cdot \text{op}[2]' \cdot \text{op}[1]' \cdot \text{op}[0]'$

$\text{addu} = \text{Rtype} \cdot \text{funct}[5] \cdot \text{funct}[4]' \cdot \text{funct}[3]' \cdot$   
 $\text{funct}[2]' \cdot \text{funct}[1]' \cdot \text{funct}[0]$

	Op	Funct
LW	100011	
SW	101011	
ADDU	000000	100001
SUBU	000000	100011
ORI	001101	
LUI	001111	
BEQ	000100	
JAL	000011	

# 综合信号：第2步

- 给状态机分配寄存器

  - S0~S9：4个寄存器， fsm[3:0]

- 定义状态编号

- 用变量表达状态

$s0 = fsm[3]' \cdot fsm[2]' \cdot fsm[1]' \cdot fsm[0]'$

$s1 = fsm[3]' \cdot fsm[2]' \cdot fsm[1]' \cdot fsm[0]$

$s2 = fsm[3]' \cdot fsm[2]' \cdot fsm[1] \cdot fsm[0]'$

...

$s8 = fsm[3] \cdot fsm[2]' \cdot fsm[1]' \cdot fsm[0]'$

$s9 = fsm[3] \cdot fsm[2]' \cdot fsm[1]' \cdot fsm[0]$

状态名	编号
S0	0000
S1	0001
S2	0010
S3	0011
S4	0100
S5	0101
S6	0110
S7	0111
S8	1000
S9	1001

# 综合信号：第3步(以PCW<sub>r</sub>为例)

	Op	Funct	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
LW	100011		1	0	0	0	0	0	0	0	0	0
SW	101011		1	0	0	0	0	0	0	0	0	0
ADDU	000000	100001	1	0	0	0	0	0	0	0	0	0
SUBU	000000	100011	1	0	0	0	0	0	0	0	0	0
ORI	001101		1	0	0	0	0	0	0	0	0	0
LUI	001111		1	0	0	0	0	0	0	0	0	0
BEQ	000100		1	0	0	0	0	0	0	0	0/1	0
JAL	000011		1	0	0	0	0	0	0	0	0	1

$$\begin{aligned} \text{PCW}_r = & (\text{lw} + \text{sw} + \text{addu} + \text{subu} + \text{ori} + \text{lui} + \text{beq} + \text{jal}) \cdot \text{S0} + \\ & \text{beq} \cdot \text{zero} + \\ & \text{jal} \cdot \text{s9} \end{aligned}$$

# 合并

- 构造出N类表

- $N \ll 56!$

- 示例：PCWr

- 抽取：N张表分别抽取PCWr的所有真值

- 真值：形成PCWr的真值表

- 方程：真值表化简

注意：

⇒ 某些信号(ALUOp)可能需要二次真值表

ADD

SW

LW

	Op	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr		1	0					0	0		

	Op	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr		1	0	0		0					

	Op	S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
PCWr		1	0	0	0	0					
IRWr		1	0	0	0	0					
RFDatSrc	01										
RegDst	00										
ExtOp	S										
RegWr		0	0	0	0	1					
ALUSrcA		00	X	1	X	X					
ALUSrcB		01	X	10	XX	XX					
ALUOp		00	X	00	XX	XX					
PCSrc		00	X	XX	XX	XX					
MemWr		0	0	0	0	0					

学计算机学院

# 提纲

- 内容主要取材
  - 数字设计和计算机体系结构（第3章，第7章）
- 多周期数据通路控制信号分析
- 多周期控制器状态机构造
- 多周期性能分析



# Review: Processor Performance


## Program Execution Time

$$= (\text{\#instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \text{\# instructions} \times \text{CPI} \times T_c$$

**CPI: Cycle/instruction**

# Single-Cycle Performance

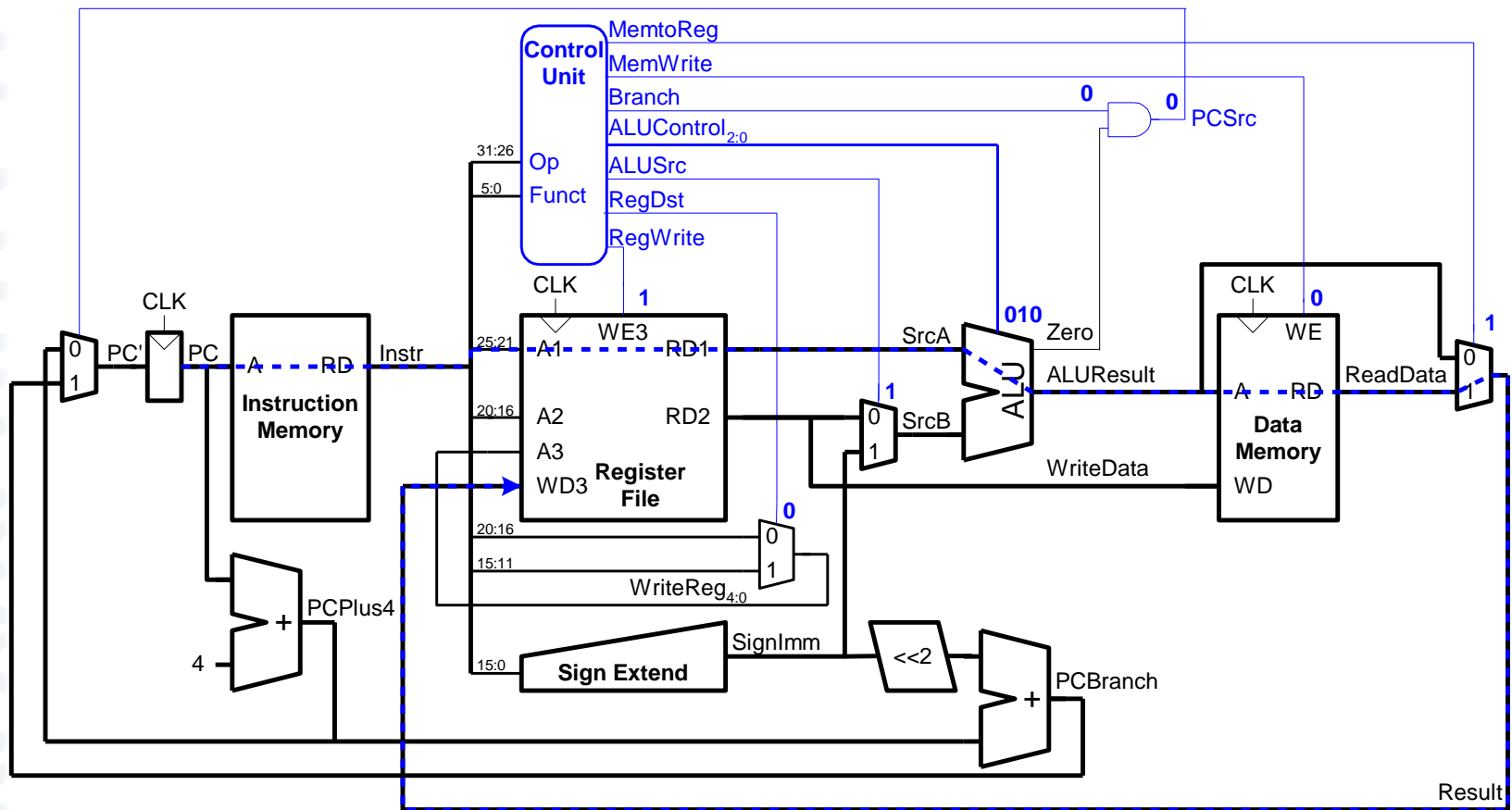

$T_C$  limited by critical path (1w)

# Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq\_PC} + t_{mem} + \max(t_{RFread}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- Typically, limiting paths are:

- memory, ALU, register file

- $T_c = t_{pcq\_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$

# Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$T_c = ?$$

# Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq\_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\&= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\&= 925 \text{ ps}\end{aligned}$$

# Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= \mathbf{92.5 \text{ seconds}}\end{aligned}$$

# Multicycle Processor Performance


- Instructions take different number of cycles:
  - 3 cycles: beq, j
  - 4 cycles: R-Type, sw, addi
  - 5 cycles: lw
- CPI is weighted average
- SPECINT2000 benchmark:
  - 25% loads
  - 10% stores
  - 11% branches
  - 2% jumps
  - 52% R-type

**Average CPI** =  $(0.11 + 0.2)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$
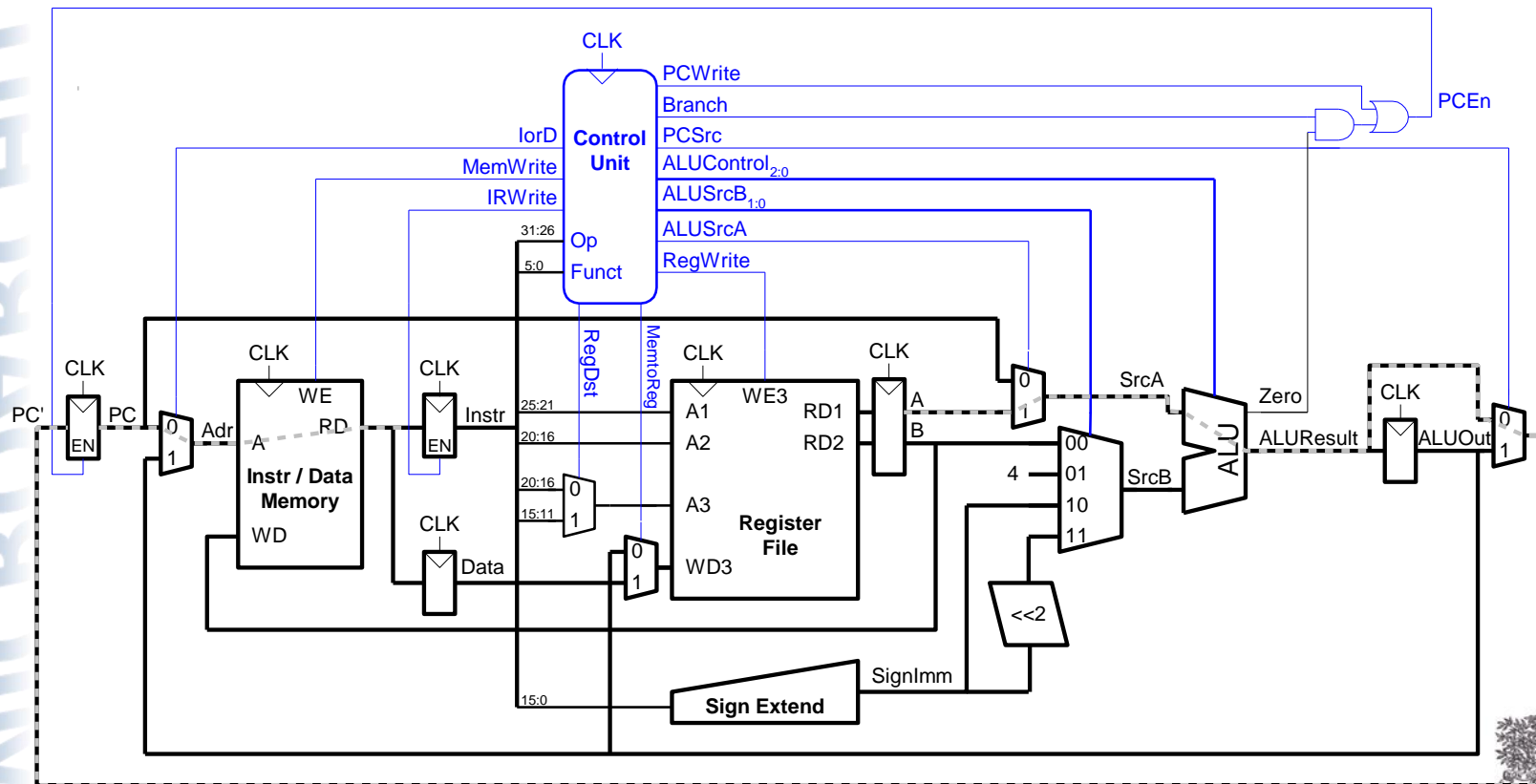
# Multicycle Processor Performance

Multicycle critical path:

$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$





# Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$T_c = ?$$

# Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq\_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\&= t_{pcq\_PC} + t_{mux} + t_{mem} + t_{setup} \\&= [30 + 25 + 250 + 20] \text{ ps} \\&= \mathbf{325 \text{ ps}}\end{aligned}$$

# Chapter 7 :: Topics

- For a program with 100 billion instructions executing on a multicycle MIPS processor
  - $CPI = 4.12$
  - $T_c = 325 \text{ ps}$

Execution Time =

- For a program with 100 billion instructions executing on a multicycle MIPS processor
  - $\text{CPI} = 4.12$
  - $T_c = 325 \text{ ps}$

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= 133.9 \text{ seconds}\end{aligned}$$

- This is **slower** than the single-cycle processor (92.5 seconds). Why?

# Multicycle Performance Example

Program with 100 billion instructions

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= \mathbf{133.9 \text{ seconds}}\end{aligned}$$

This is **slower** than the single-cycle processor (92.5 seconds). Why?

- Not all steps same length
- Sequencing overhead for each step ( $t_{pcq} + t_{\text{setup}} = 50 \text{ ps}$ )

